

Advanced Digital Design Lab 5


Diego Deoliveira

Part I: 8bit Accumulator Logisim Circuit

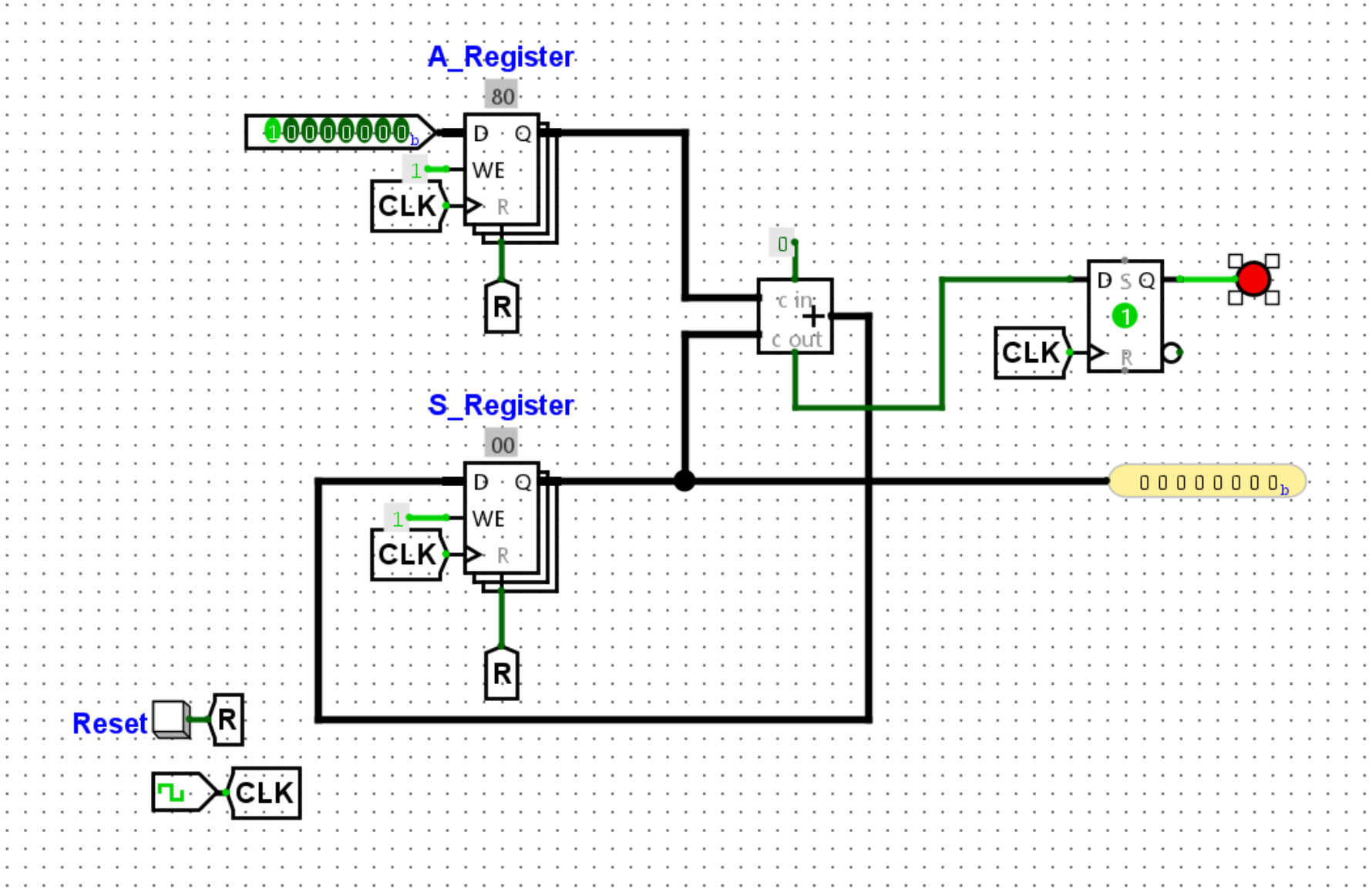


Part I: RTL Viewer Accumulator & Debounce

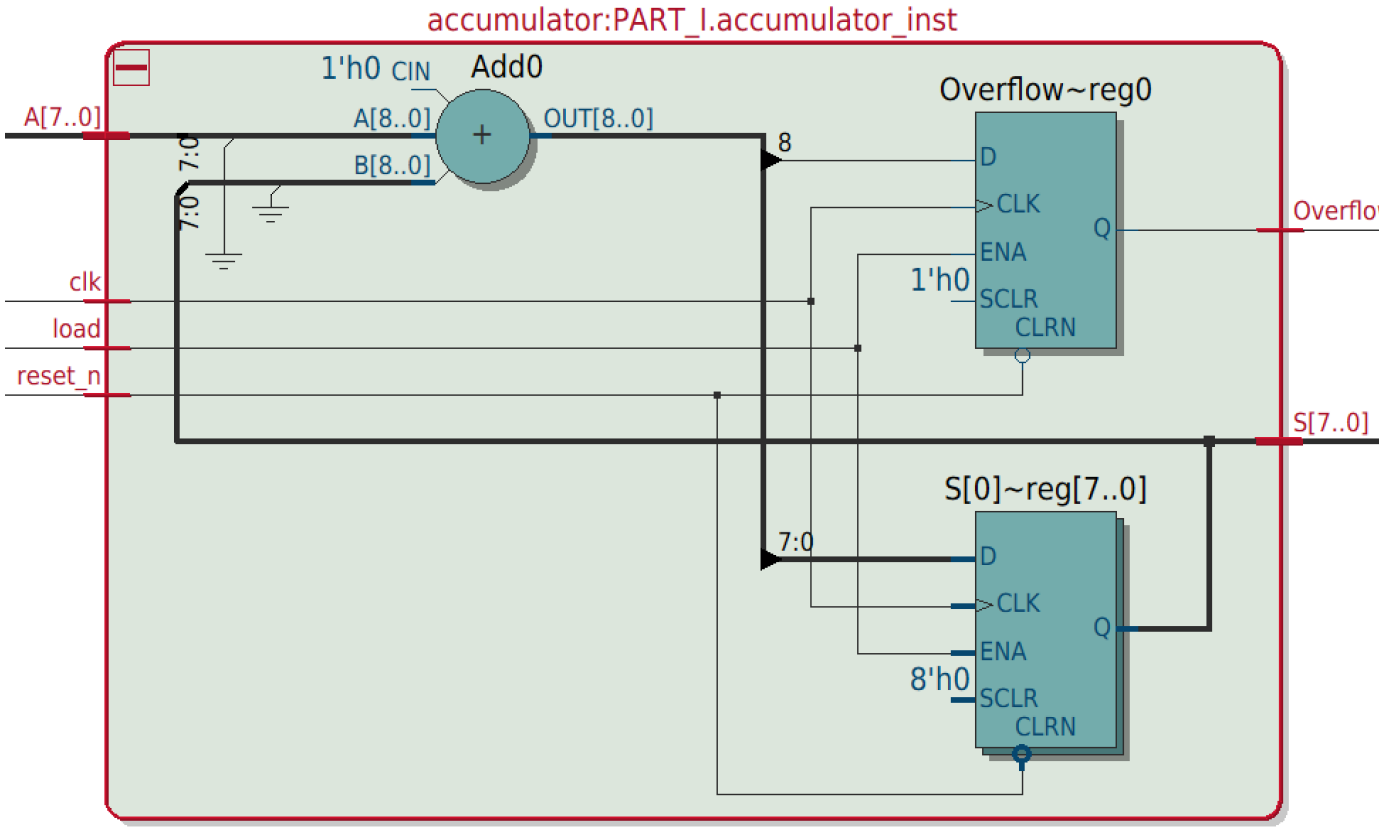


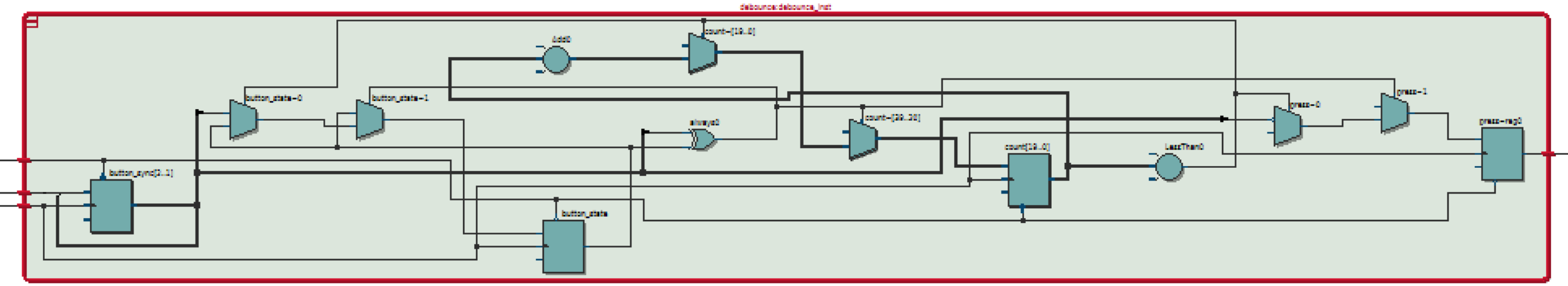


Part II: 8bit Accumulator/Subtractor Logisim Circuit

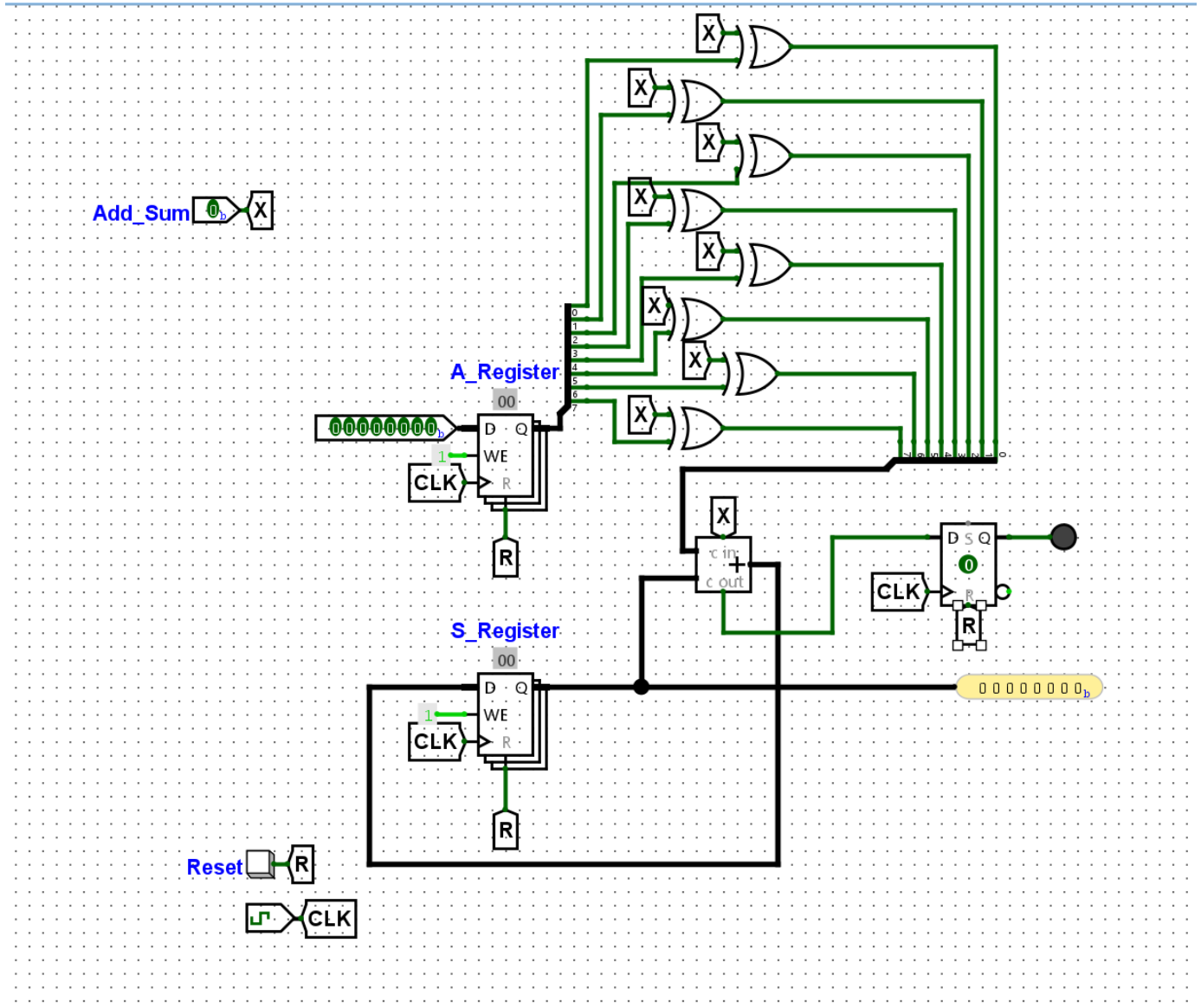


Part II: RTL Viewer Accumulator/Subtractor

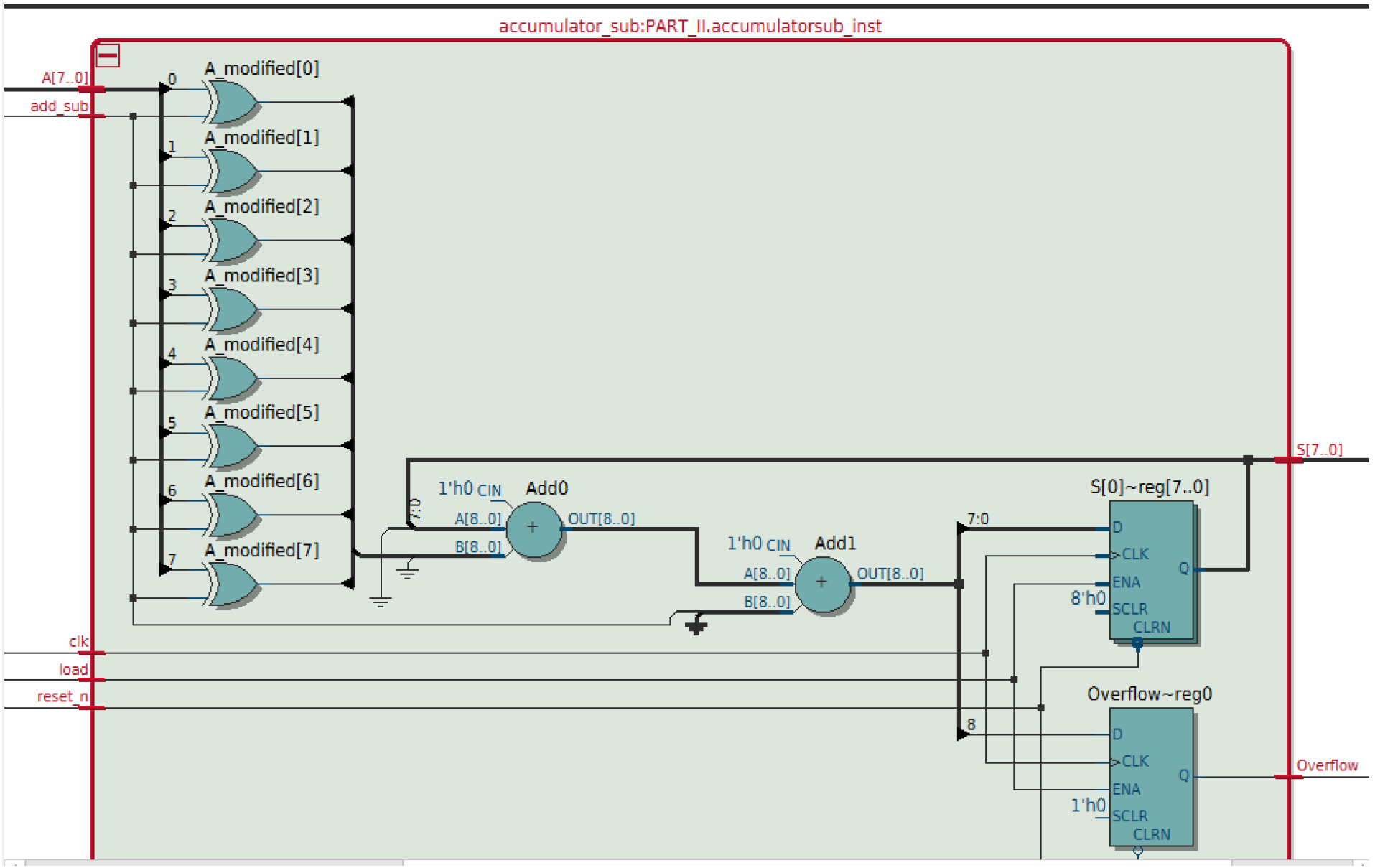


Part III: Multiplier Logisim Circuit

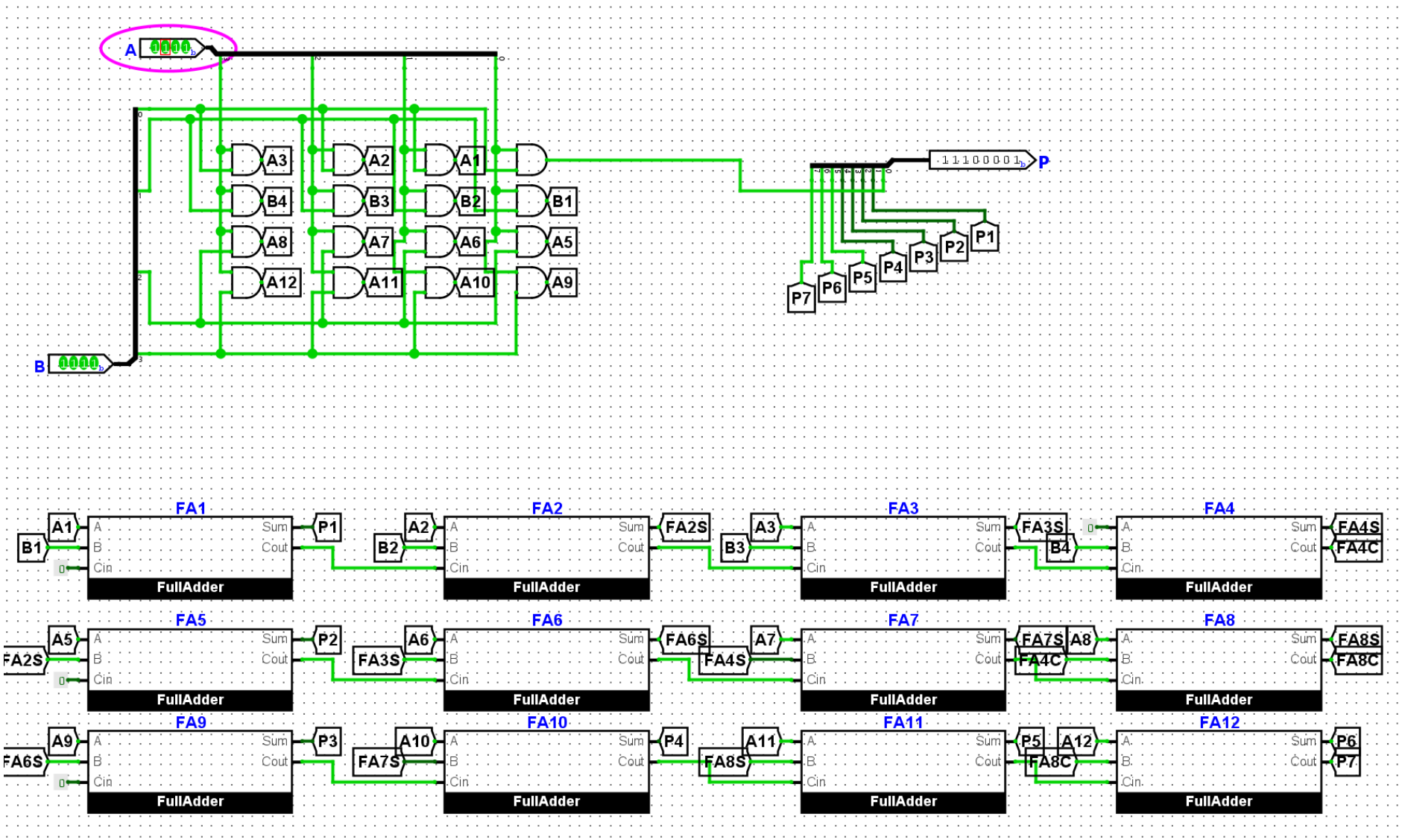


Part III: Multiplier RTL Viewer 4x4 Multiplier & Hex Decoder

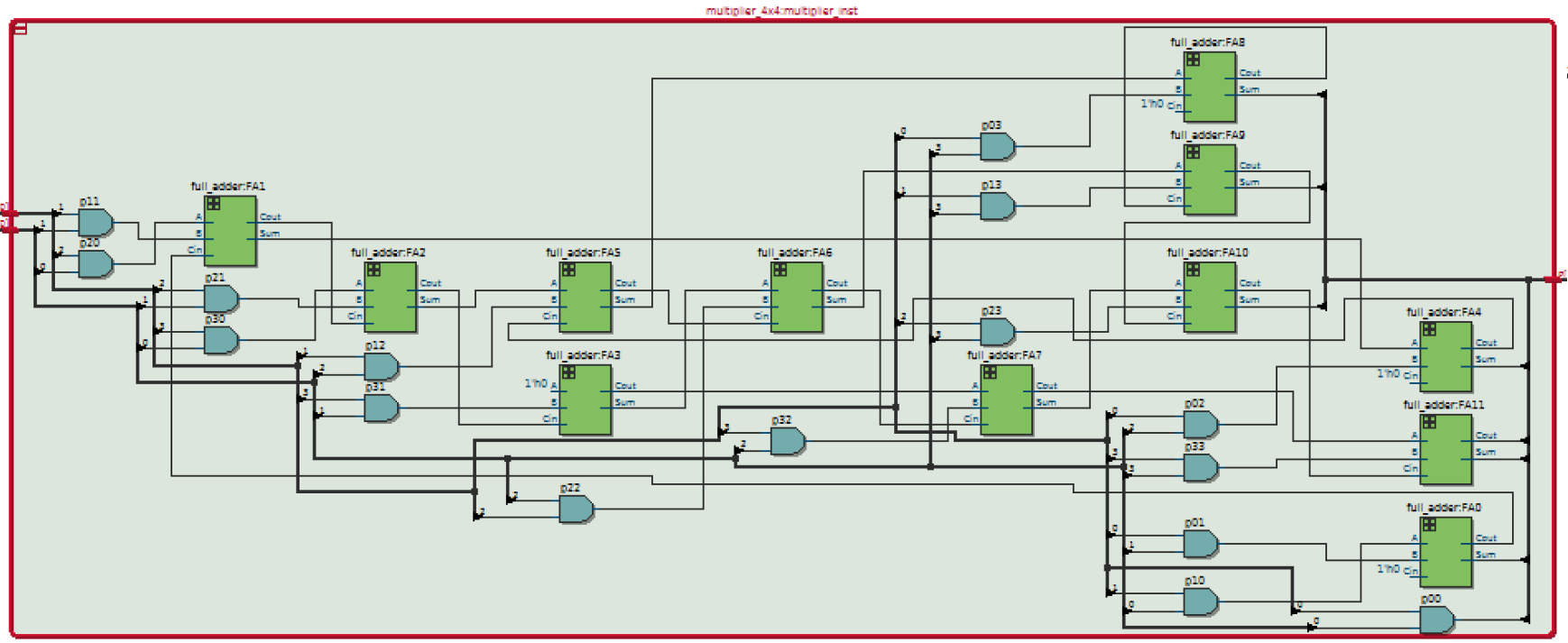


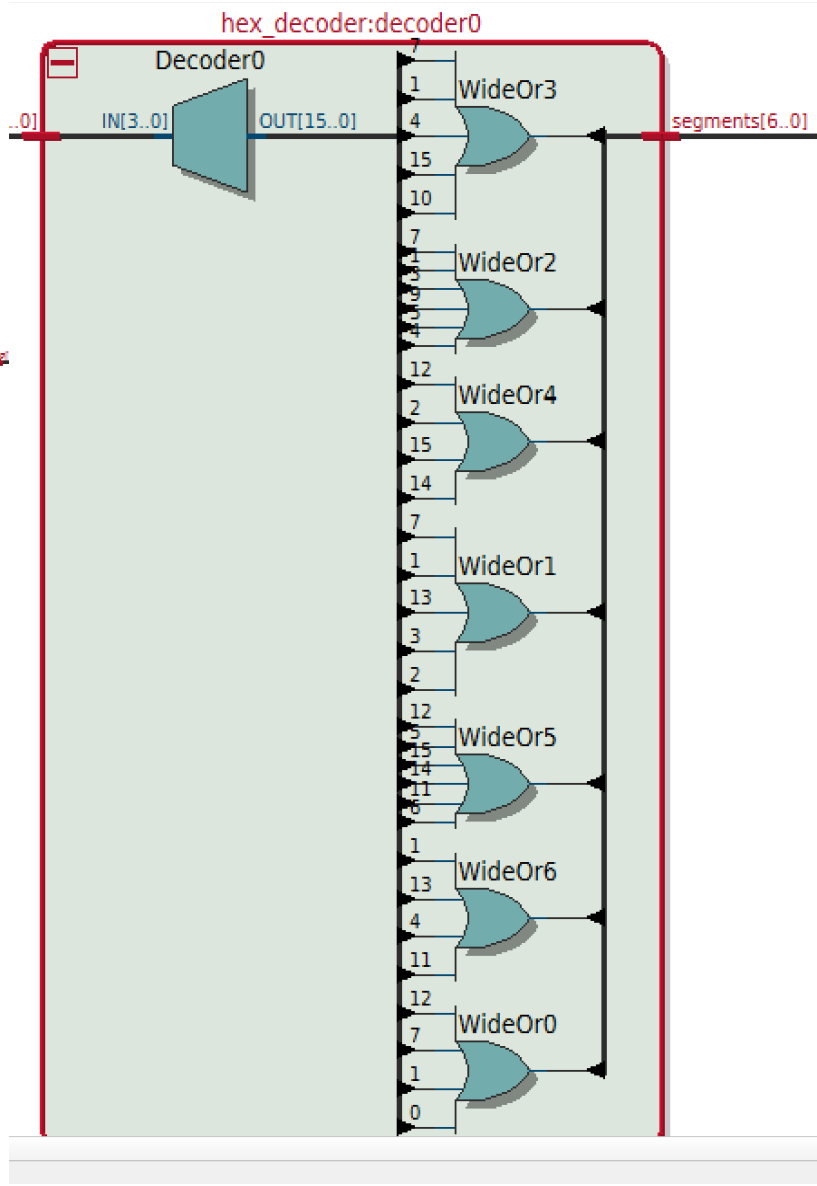


Part IV: RTL Viewer Top View

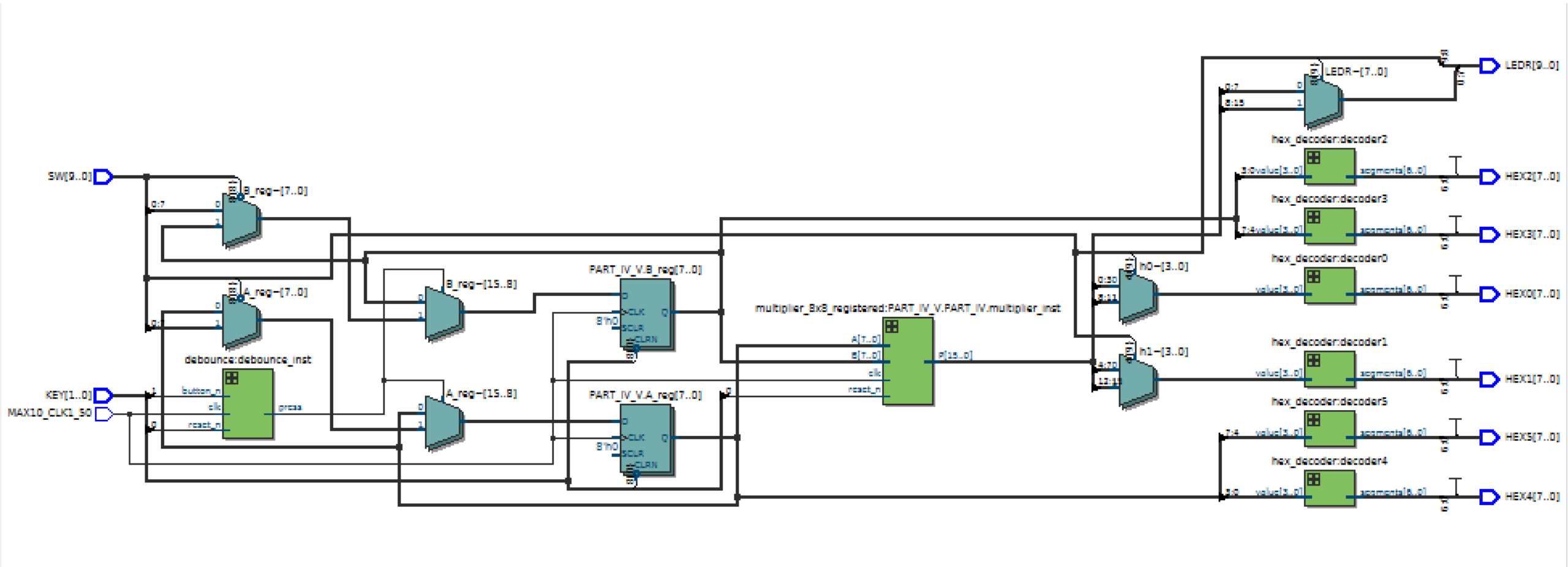



Part IV: RTL Viewer 8x8 Registered Multiplier

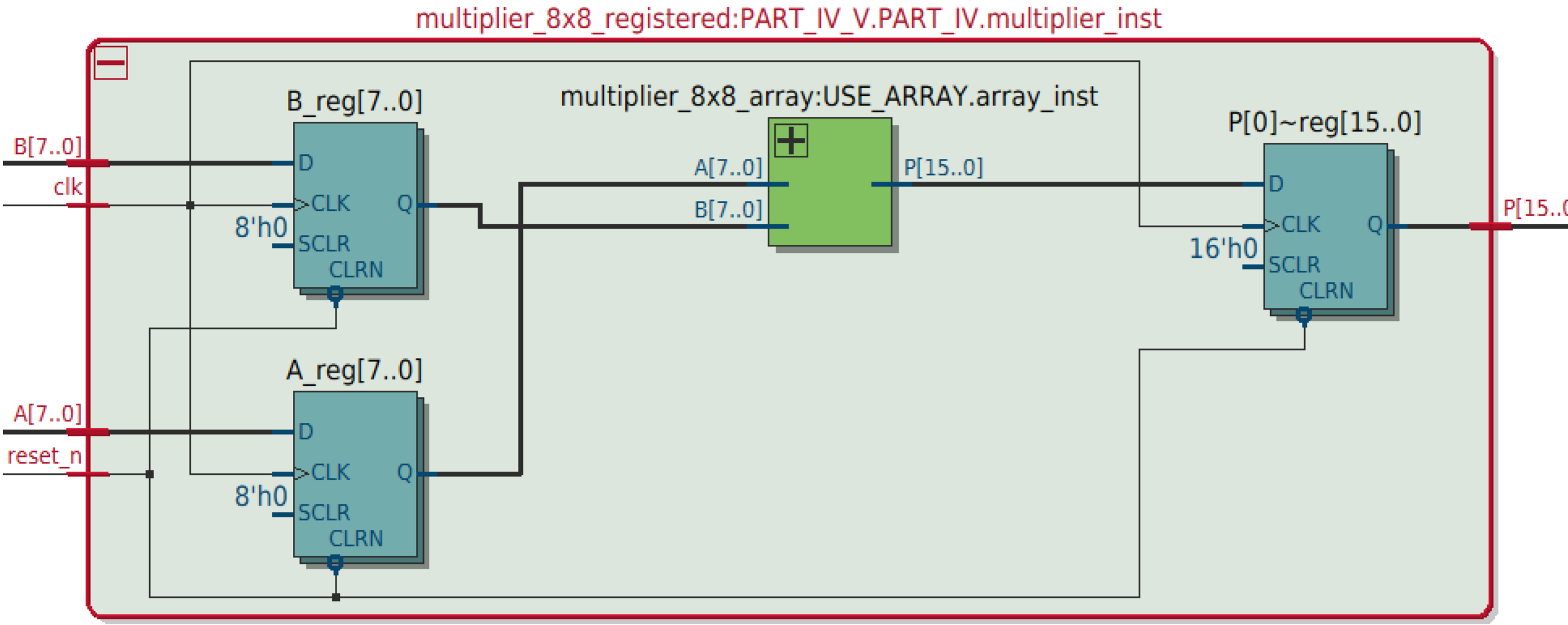

Part IV: RTL Viewer 8x8 Multiplier using Sequential Additions & Partial Product Generator & 16 Bit Adder

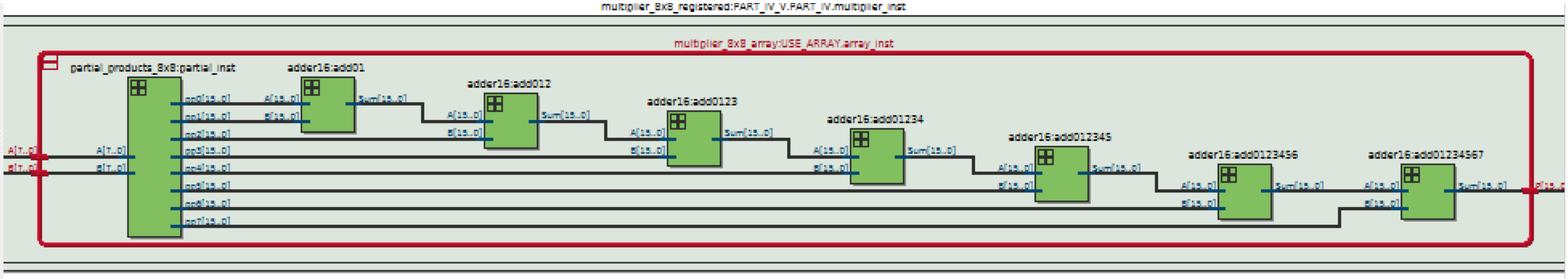

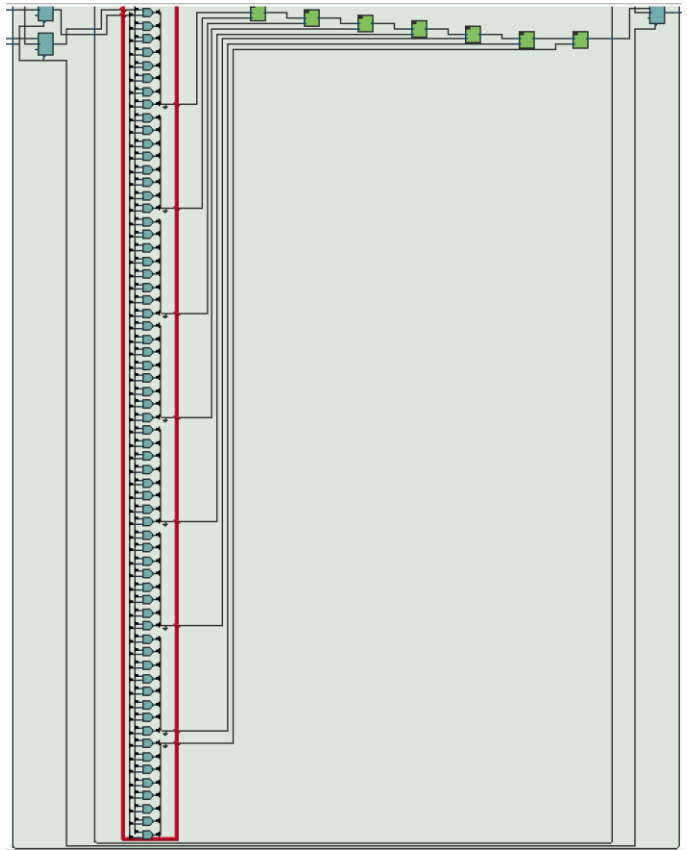

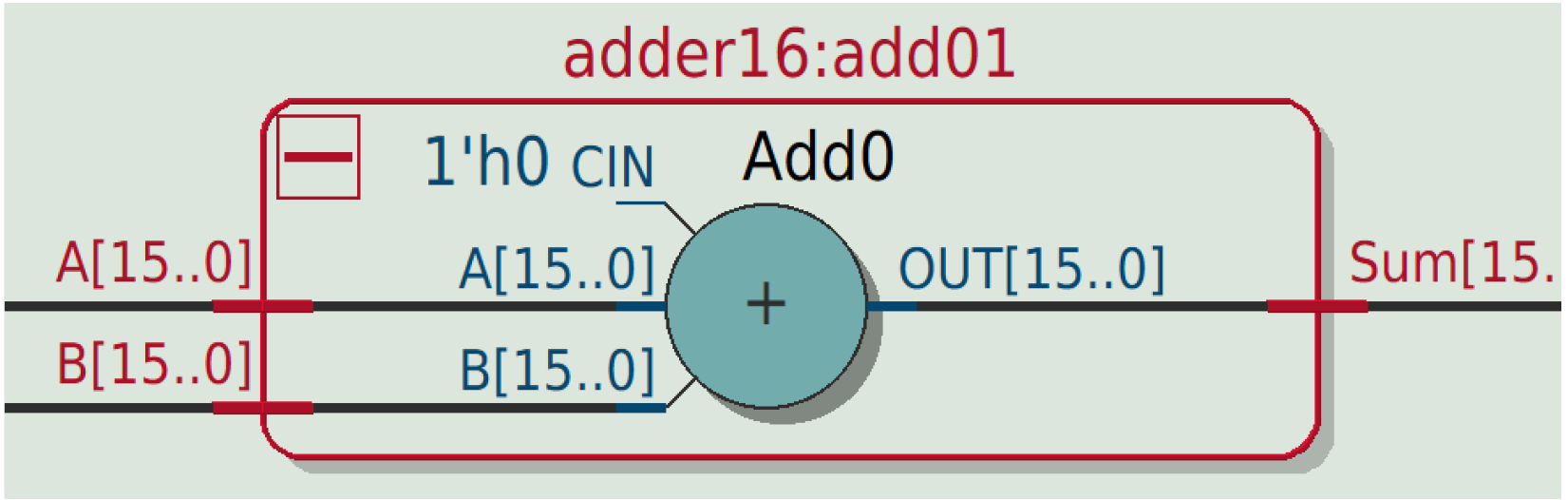

Part V: RTL Viewer Top View

